

## ***AN-1796 LMP7721 Evaluation Board***

---


---

---

### **1 Introduction**

The LMP7721 evaluation board provides a platform to test the input bias current and performance of the LMP7721 amplifier. The LMP7721 amplifier is optimized for ultra low input bias current, 3 fA typical, by using on chip guard drivers and a package pin out to isolate the amplifier's inputs from its power supply and output pins.

[Figure 1](#) is the schematic diagram for the LMP7721 evaluation board.

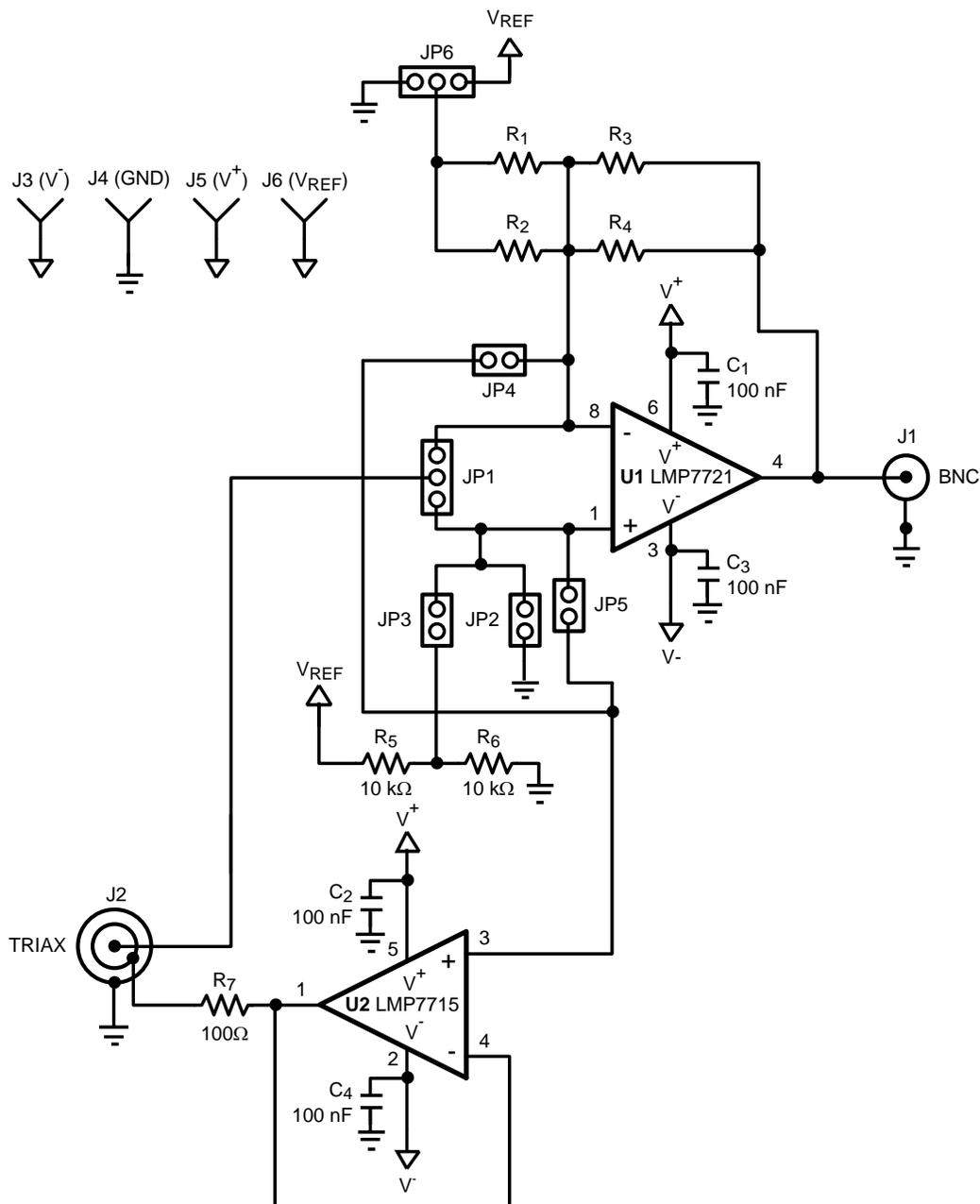
**Figure 1. LMP7721 Evaluation Board**

The evaluation board is design to be compatible with the 1 fA input bias current of the LMP7721 by providing a guarded area around the input puts of the amplifier. The input guard creates an equal potential zone around the input pins that prevents leakage currents from other parts of the printed circuit board (PCB) from reaching the input pins and causing an error current. A description of the board's features is discussed in the following secitons.

## 2 Power Supply Connections

J3, J4 and J5 are the power supply connections. The power supply can be a single supply with a range 1.8 to 5.5 V. Also, a split supply voltage can be used with the with the condition that  $1.8\text{ V} \leq V^+ - (V^-) \leq 5.5\text{ V}$ .

For single supply operation, J3 and J4 are connected together and is the ground connection. The positive supply voltage connection is J5.

For split-supply operation, the negative supply voltage is connected to J3. The positive supply voltage is connected to J5 and the ground (or common) connection of the supplies is connected to J4.

### 3 Reference Voltage Connection ( $V_{REF}$ )

The LMP7721 can be configured as an inverting amplifier or a non-inverting amplifier. In each case, it may be required to provide a level shift voltage to keep the output voltage within a specified range and is accomplished by using the  $V_{REF}$  connection. Jumper JP3 is used to connect the  $V_{REF}$  to the non-inverting input of U1 when U1 is used in an inverting amplifier configuration. Jumper JP6 is used to connect the  $V_{REF}$  to the inverting input of U1 when U1 is used in a non-inverting amplifier configuration.

### 4 Components $R_1$ , $R_2$ , $R_3$ , $R_4$ , $R_5$ , $R_6$ and $R_7$

These components are shown as resistors on the schematic, but are not mounted on the board. This evaluation board uses pin sockets at the location of these components to give you the freedom to configure the LMP7721 amplifier to best fit the application being considered.

### 5 Jumper Functions

**JP1**— JP1 is used to connect the signal terminal of the triax connector (J2) to the inverting input or the non-inverting input of U1, the LMP7721 amplifier.

**JP2**— JP2 is used to connect the non-inverting input of U1 to ground.

**JP3**— JP3 is used to connect the non-inverting terminal of the LMP7721 to the  $V_{REF}$  voltage. The connection to  $V_{REF}$  can be direct by using a wire jumper in the position of  $R_5$ , or through a voltage divider by using resistors in the positions of  $R_5$  and  $R_6$ .

**JP4**— JP4 is used to connect the guard and guard driver to the inverting terminal of the LMP7721 when it is the low impedance node. This is the case when the LMP7721 is used as a non-inverting amplifier.

**JP5**— JP5 is used to connect the guard and guard driver to the non-inverting terminal of the LMP7721 when it is the low impedance node. This is the case when the LMP7721 is used as an inverting amplifier.

**JP6**— JP6 is used to connect the inverting terminal of the LMP7721 to the  $V_{REF}$  voltage or to ground. This is used when U1 is used as a non-inverting amplifier.

### 6 Input and output connectors

**J1**— J1 is a BNC connect and is the output of the LMP7721 amplifier


**J2**— J2 is a Triax connector and is used to connect a signal source to the input of the LMP7721. This component is not mounted on the board. A Triax connector is similar to a BNC connector but includes a shield between the central conductor and the outer shield and is referred to as a guard. A guard driver drives the guard to the same voltage as the center conductor, which minimizes any leakage currents in the connector or in the triax cable connected to it.

### 7 Example Applications

Non-inverting amplifier with a gain of two:

In this example, a sensor such as a pH electrode is the signal source and the LMP7721 is being used to buffer and amplify the signal. The output of a pH electrode, at 25°C ranges from about +415 mV to -415 mV as the pH ranges from 0 to 14. The output impedance of a pH electrode is extremely high, greater than 5 to 10 M $\Omega$ , so the LMP7721 is an excellent amplifier to buffer the output of a pH electrode.

For this application, a  $\pm 2.5$  V supply voltage is used. Figure 2 shows the placement of the jumpers and components.

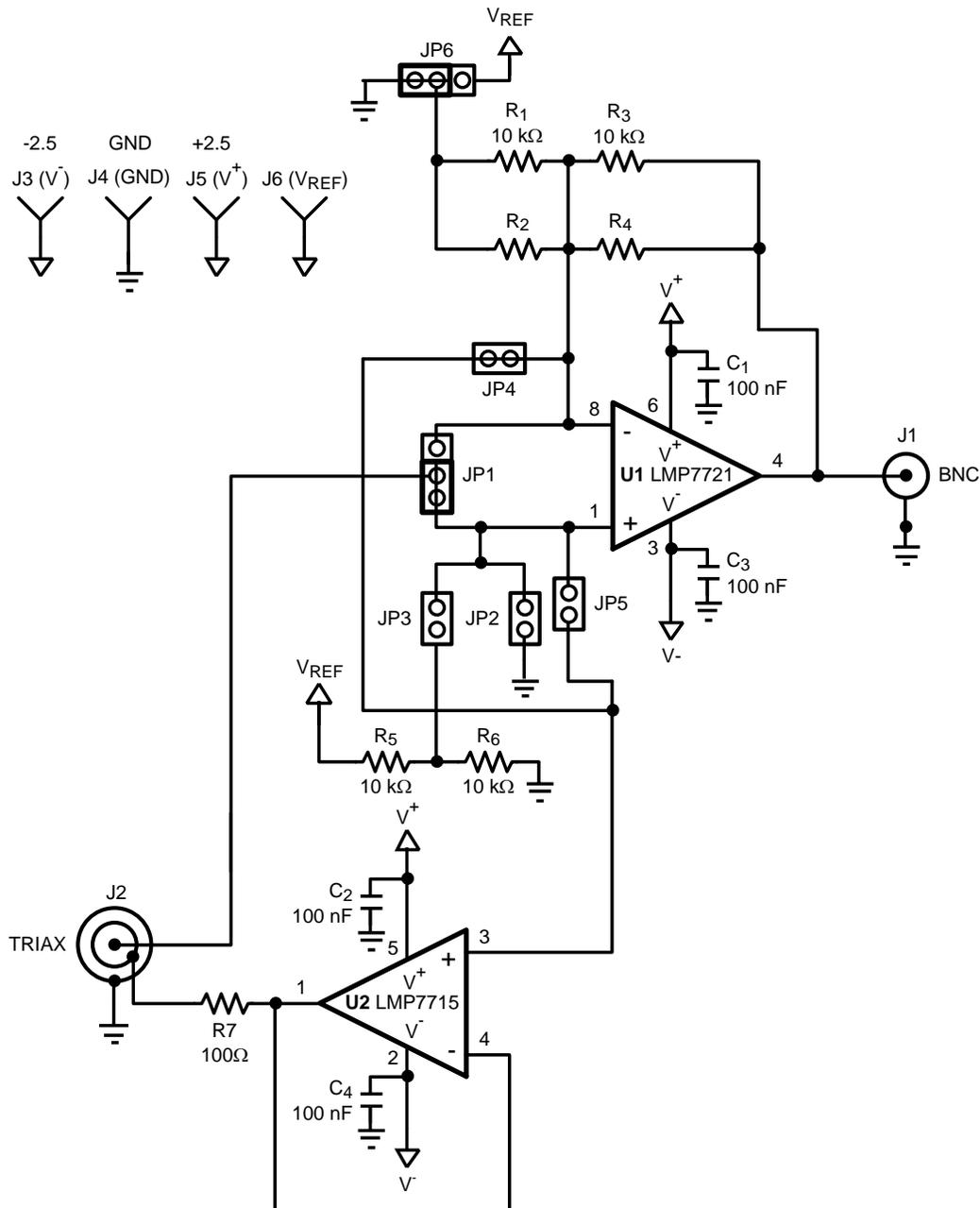

**Figure 2. Schematic Showing Placement of Jumpers and Components**

## 8 Transimpedance Amplifier (Inverting Amplifier With Level Shift)

In this application, the LMP7721 is used as a transimpedance amplifier that converts the current generated in the pin diode by light, or other radiation source, to a voltage at the amplifier's output. The input is biased to 2.5 V by the  $V_{REF}$  and the resistive divider  $R_5$  and  $R_6$ . Current from the pin diode generates a voltage at the amplifier's output equal to  $(2.5 \text{ V} - (I_{\text{pin-diode}}) \times (R_3))$ .

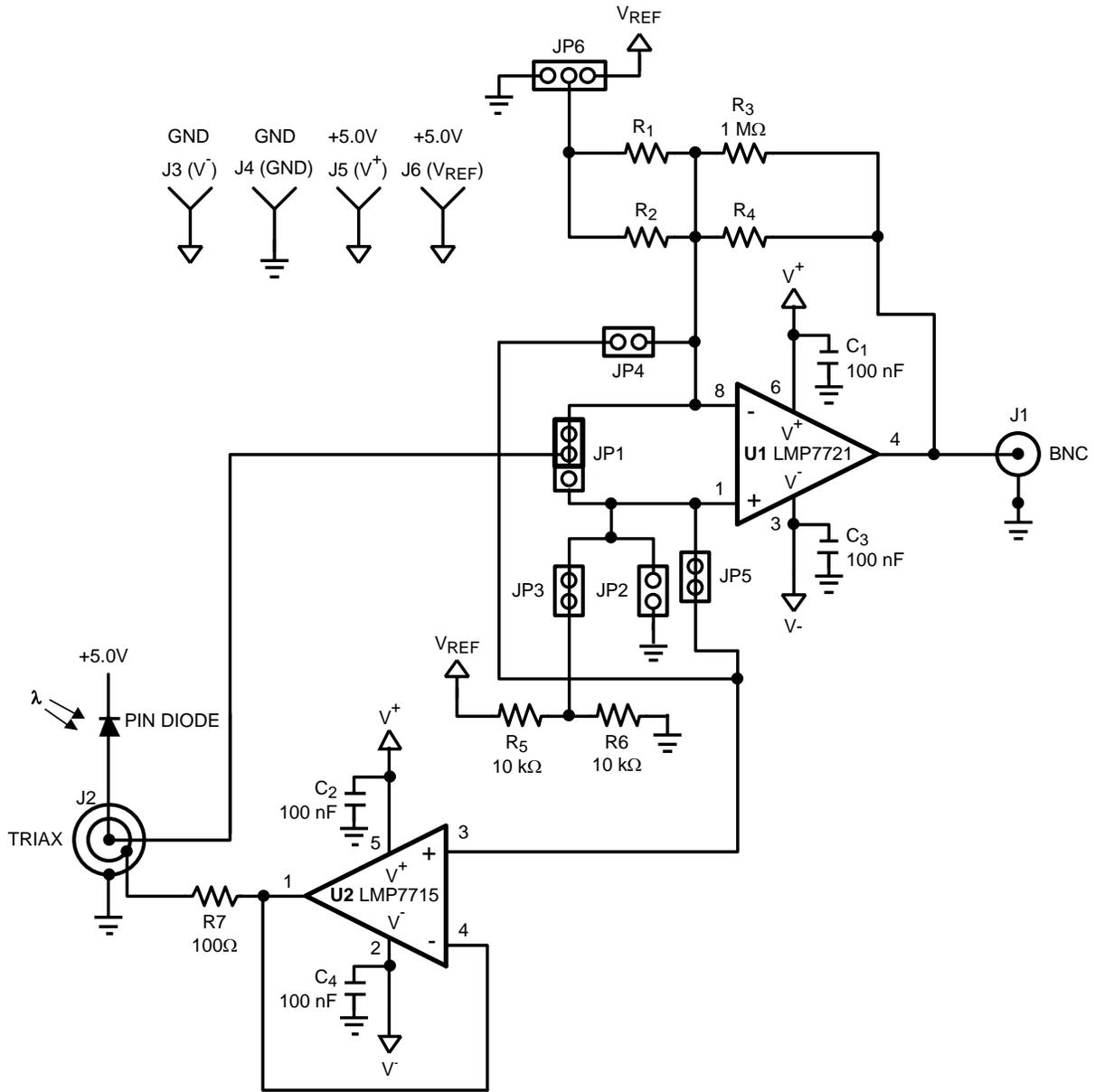


Table 1 shows the Bill of Material (BOM) of the evaluation board.

**Table 1. Bill of Material (BOM)**

<b>Designator</b>	<b>Description</b>	<b>Comment</b>
J5	Jack connector	Red
J3	Jack connector	Green
J4	Jack connector	Black
J6	Jack connector	Yellow
C1 –C4	0805 capacitor	100 nF
J1	BNC	
JP1, JP6	3 pin header	
JP2 –JP5	2 pin header	
U1	LMP7721	8-Pin SOIC
U2	LMP7715	5-Pin SOT-23
R1 – R7	Leaded resistor	Not stuffed
J2	Triax connector	Not stuffed
No Designator	PC pin receptacle	For R1 – R7
No Designator	1/2", 4–40 nylon threaded standoff	Qty. 4
No Designator	3/8", 4–40 Screw	Qty. 4

## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, enhancements, improvements and other changes to its semiconductor products and services per JESD46, latest issue, and to discontinue any product or service per JESD48, latest issue. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All semiconductor products (also referred to herein as "components") are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its components to the specifications applicable at the time of sale, in accordance with the warranty in TI's terms and conditions of sale of semiconductor products. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by applicable law, testing of all parameters of each component is not necessarily performed.

TI assumes no liability for applications assistance or the design of Buyers' products. Buyers are responsible for their products and applications using TI components. To minimize the risks associated with Buyers' products and applications, Buyers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right relating to any combination, machine, or process in which TI components or services are used. Information published by TI regarding third-party products or services does not constitute a license to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of significant portions of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI components or services with statements different from or beyond the parameters stated by TI for that component or service voids all express and any implied warranties for the associated TI component or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

Buyer acknowledges and agrees that it is solely responsible for compliance with all legal, regulatory and safety-related requirements concerning its products, and any use of TI components in its applications, notwithstanding any applications-related information or support that may be provided by TI. Buyer represents and agrees that it has all the necessary expertise to create and implement safeguards which anticipate dangerous consequences of failures, monitor failures and their consequences, lessen the likelihood of failures that might cause harm and take appropriate remedial actions. Buyer will fully indemnify TI and its representatives against any damages arising out of the use of any TI components in safety-critical applications.

In some cases, TI components may be promoted specifically to facilitate safety-related applications. With such components, TI's goal is to help enable customers to design and create their own end-product solutions that meet applicable functional safety standards and requirements. Nonetheless, such components are subject to these terms.

No TI components are authorized for use in FDA Class III (or similar life-critical medical equipment) unless authorized officers of the parties have executed a special agreement specifically governing such use.

Only those TI components which TI has specifically designated as military grade or "enhanced plastic" are designed and intended for use in military/aerospace applications or environments. Buyer acknowledges and agrees that any military or aerospace use of TI components which have **not** been so designated is solely at the Buyer's risk, and that Buyer is solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI has specifically designated certain components as meeting ISO/TS16949 requirements, mainly for automotive use. In any case of use of non-designated products, TI will not be responsible for any failure to meet ISO/TS16949.

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Applications Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Automotive and Transportation	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

### TI E2E Community

[e2e.ti.com](http://e2e.ti.com)